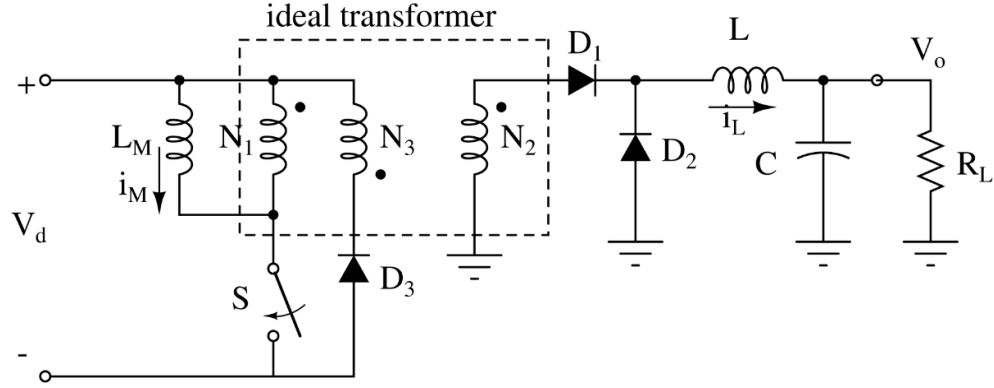



EE419/519 Homework Assignment #4

Due December 17, 2024

- Consider the following converter. S is ON for $D_1 T_s$. The capacitor, C , is sufficiently large so that the output ripple is negligible. Ignore the voltage drop of the diodes. We have $V_d=300V$, $L=100\mu H$, $L_M=1.5mH$, and $T_s=40\mu s$.



- Assuming that i_L is always greater than 0, choose N_1 , N_2 , and D to have $V_o=12V$.
 - Find the maximum value of R_L to ensure a continuous mode of operation.
 - Choose a value for N_3 to have i_M go to zero $4\mu s$ before the end of the cycle.
 - Choose a load resistance R_L larger than the maximum value. Determine the output voltage under this condition. Note that the average value of i_L is equal to V_o/R_L .
- The converter below has $V_d=200V$, D , $T_s=40\mu s$. S_1 and S_2 are ON consecutively for a duty cycle of $D<0.5$. S_1 turns on at the beginning of the cycle, and S_2 turns on at the half-point of the cycle. The capacitor, C , is sufficiently large so that the output ripple is negligible. Ignore the voltage drop of the diodes. The inductors are $L_M=18mH$ and $L=100\mu H$.

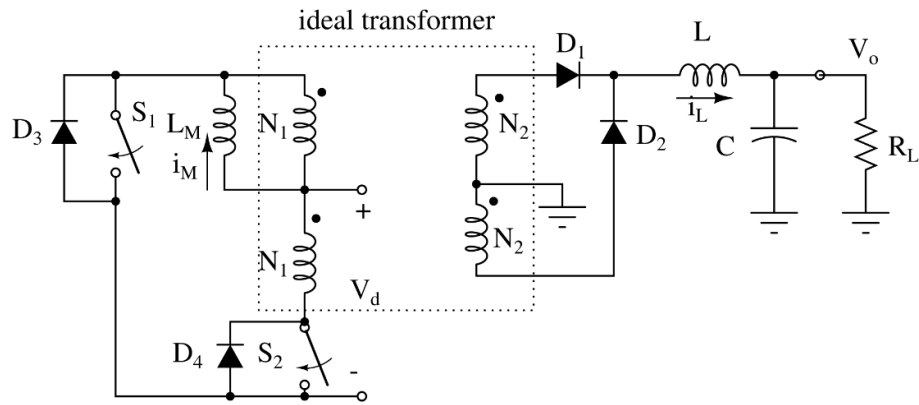

- Assume that both diodes D_1 and D_2 are ON during the time switches are off. Choose N_1 , N_2 , and D to have $V_o=18V$.
- Find the maximum value of R_L to ensure this mode of operation by plotting the i_L for the boundary case. Note that during the time switches are both off, to assure that both D_1 and D_2 are ON, $i_L(t)$ should be greater than $(N_1/2N_2)V_d D T_s / L_M$.
- Plot the diode currents i_{D1} and i_{D2} for the boundary case.