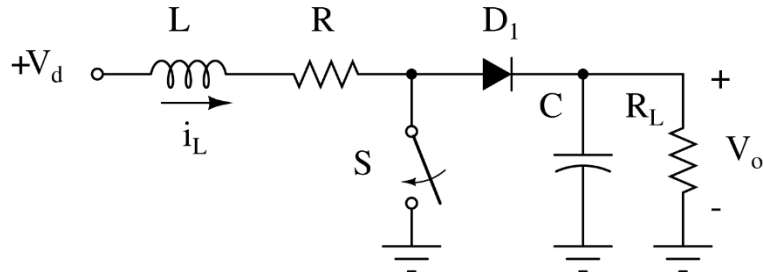


EE419/519 Homework Assignment #3 (v2)

Due November 17, 2024

1. Consider the following Boost converter with $V_d=12\text{V}$, $L=100\mu\text{H}$, $R=1\Omega$, $D=0.5$, $T_s=40\mu\text{s}$. The diode has a forward voltage drop of 0.8V when conducting. The capacitor C is sufficiently large so that the output ripple is negligible.



- i. In PSS, $i_L(0)=0.1+\text{mod}(\text{BilkentID},10)/10$. Find the output voltage V_o . Note that the inductor current follows an exponential curve: $i_L(t)=i_{L\text{final}}+(i_{L\text{initial}}-i_{L\text{final}})e^{-t/\tau}$ rather than a linear ramp.
 - ii. Find the value of the load resistance R_L by finding the average value of the **diode** current.
 - iii. Find the peak-to-peak ripple at the output if the capacitor, C , has an ESR of 0.01Ω .
2. A flyback converter has $V_d=200\text{V}$, $D=0.05+\text{mod}(\text{BilkentID},5)/20$, $T_s=40\mu\text{s}$. The transformer has $L_M=1200\mu\text{H}$, $L_L=100\mu\text{H}$, and $N_1/N_2=2+\text{mod}(\text{BilkentID},5)$.
 - a. Find the output voltage if $\Delta_2=0.7$.
 - b. Find the Zener diode voltage of the snubber network if $\Delta_1=0.02$.
 - c. Find the power dissipated in the snubber network.
 - d. Find the value of the output load resistance.