

Bengisu Müntehe Koç

21801974

EEE 419 – 01

13.11.2024

EEE 419 Power Electronics Project: Flyback Converter

Introduction

The objective of this project is to design a DC-DC flyback converter using MC34063A which converts the 12V input voltage to 25V output voltage.

Flyback converter is a type of DC-DC converter which operates in periodic steady state (PSS). It is used in applications where electrical isolation between input and output is needed. It can step up or down the input voltage. The simple schematic of flyback converter is shown in Figure 1.

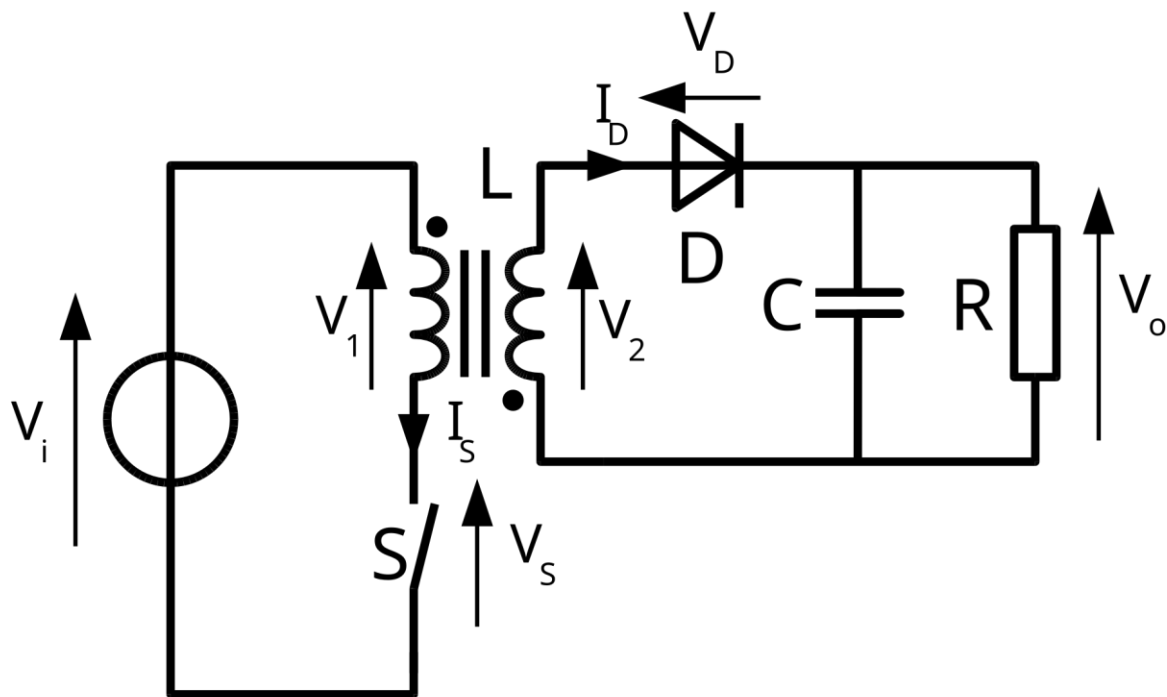


Figure 1: Simple Schematic of Flyback Converter [1]

The flyback converter functions by utilizing a transformer to store and transfer energy in a pulsed manner, enabling electrical isolation and versatile voltage conversion. In the "on" state, a switch (typically a transistor) closes, allowing current to flow through the primary winding of the transformer. This current flow generates a magnetic field, which stores energy within the transformer core. When the switch opens (the "off" state), the magnetic field collapses, inducing a voltage in the secondary winding in the opposite direction. This induced voltage causes current to flow through a diode to the output capacitor and load, releasing the stored energy. By controlling the duty cycle of the switch, the flyback converter maintains a regulated output voltage, which can be either higher or lower than the input voltage. The converter operates efficiently in both continuous and discontinuous modes, depending on the load requirements and design configuration.

- T_s is chosen as $9\mu s$. This is the switching period of the converter.
- Since i_{peak} is given as $1.1A$, R_{SC} is calculated as

$$R_{SC} = \frac{0.33}{i_{peak}} = 0.3\Omega$$

- β_{min} is equal to 50 according to the datasheet of the MC34063A. R_C is used to supply sufficient base current for the switching transistor of MC34063A. The resistance is calculated as

$$R_C \leq \frac{\beta_{min} \cdot (V_d - 1.6)}{i_{peak}} = 472.7\Omega$$

Where V_d is input voltage, 12V. The value of this resistance is set to 330Ω to ease the implementation of the design.

- The sum of the input and Zener diode voltage should be equal to the 35V, since the maximum allowed switch voltage of the IC is 40V. Hence the Zener diode voltage is calculated as 23V.
- V_{OR} is chosen as 9V. This value represents the reflected output voltage in the flyback converter. The voltage appears on the primary side of the transformer when energy is transferred from the primary winding to the secondary winding.
- The coupling coefficient is given as $k = 0.9$. This value represents the values of the Snubber network.
- The value of $[D + \Delta_2]$ is chosen as 0.9. This value represents a combined duty cycle factor for ensuring discontinuous mode operation in the converter. Which means that the current fully discharges each cycle and helps maximize power output and stability.
- Duty cycle of the converter is calculated as

$$D = \frac{[D + \Delta_2]}{1 + \frac{V_d}{V_{OR}}} = 0.3857$$

- Δ_1 value is found with the formula

$$\Delta_1 = D \cdot \frac{V_d}{V_Z - V_{OR}} \cdot \frac{L_L}{L_M + L_L}$$

The values L_L and L_M represent the inductor values of the snubber network. The equivalents of these values are

$$L_L = 2 \cdot L_1 = 2 \cdot (1 - k) \cdot L_1$$

$$L_M = k \cdot L_1$$

Hence the value of Δ_1 is found as 0.0601.

- The inductance of the primary is found as

$$L_1 = \frac{D \cdot T_s \cdot V_d}{i_{peak}} = 37.869\mu H$$

- The turns-ratio is found as

$$\frac{N_1}{N_2} = \frac{V_{OR}}{V_o} = \frac{9}{25}$$

- The inductance of the secondary is found as

$$L_2 = \frac{L_1}{\left(\frac{N_1}{N_2}\right)^2} = 292.197\mu H$$

- The number of the turns of the primary is found as

$$N_1 = \sqrt{\frac{L_1}{A_L}} = 15.38$$

- The number of turns of the secondary is found as

$$N_2 = \sqrt{\frac{L_2}{A_L}} = 42.73$$

- The off time of the switch is calculated as

$$T_{OFF} = (1 - D) \cdot T_S = 5.53\mu s$$

- The value of the timing capacitor C_T is found from the graph shown in Figure 3. The approximate value of the capacitor is found as 2.7nF. This value may need to change after the simulation.

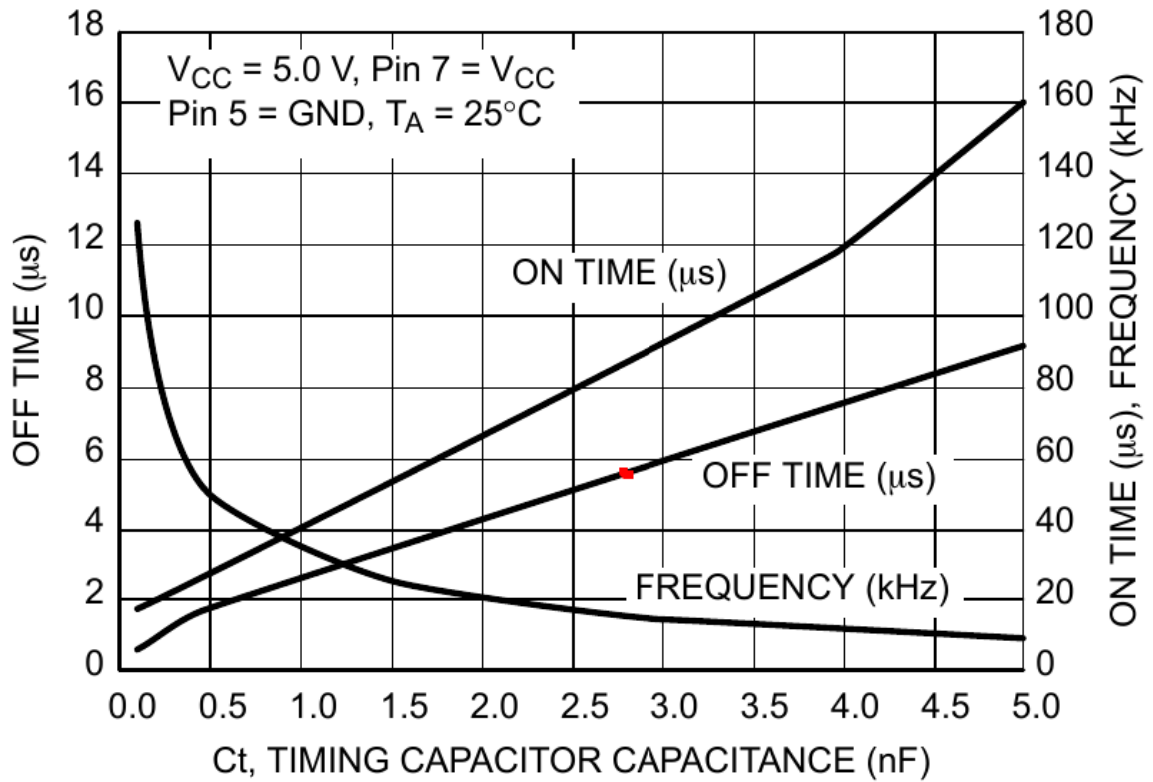


Figure 3: Graph of the Timing Capacitor Capacitance

- R_T value is given as $1M\Omega$. This resistance will not be used for implementation.
- The values of the resistances R_1 and R_2 are calculated as

$$\frac{V_O R_1}{R_1 + R_2} = 2.5V$$

This is the reference voltage of the shunt regulator. Since $R_1 + R_2$ is in the range of 50K and 150K, the values are determined as $R_1 = 10K\Omega$ and $R_2 = 90K\Omega$. In the implementation part, instead of $90K\Omega$, $82K\Omega$ will be used with a $10K\Omega$ trimpot.

- Output capacitor value is chosen as $1\mu\text{F}$ as recommended. In the implementation, this value will be increased.
- R_D value is set to 680Ω to limit the current through the photodiode.
- R_3 value is set to $10\text{K}\Omega$ to bypass the off-current of TL431.
- C_D value is set to 10nF to AC couple the cathode and feedback pins of TL431 for proper operation.
- L_3 value is set to $10\mu\text{H}$ to speed up the simulation. This inductor will be short circuited in implementation.
- R_B value is set to 220K to speed up the turn-off transient of the phototransistor.
- R_4 and R_5 values are determined as

$$1.1\text{ V} < V_d \cdot \frac{R_4}{R_4 + R_5} < 1.20\text{ V}$$

Hence the values are chosen as $R_4 = 2.2\text{K}\Omega$ and $R_5 = 22\text{K}\Omega$.

- The value of R_6 is chosen as $3.3\text{K}\Omega$ to limit the current of the phototransistor.
- Load resistance value will be determined with simulation results.
- To find the maximum theoretical output power of the converter, the output current is found as

$$I_O = \frac{1}{2} \cdot \frac{D^2 V_d^2 T_S}{(L_M + L_L)^2} \cdot \frac{N_1}{N_2} \left(\frac{L_M}{V_{OR}} - \frac{L_L}{V_Z - V_{OR}} \right)$$

Which is found to be 0.0864A , hence the output power is found to be 2.16W .

- The load resistance value is determined with simulation tests and found to be 500Ω .
- The value of timing capacitor is decreased to 680pF shorten the idle period.
- The final version of the circuit is shown in Figure 4.

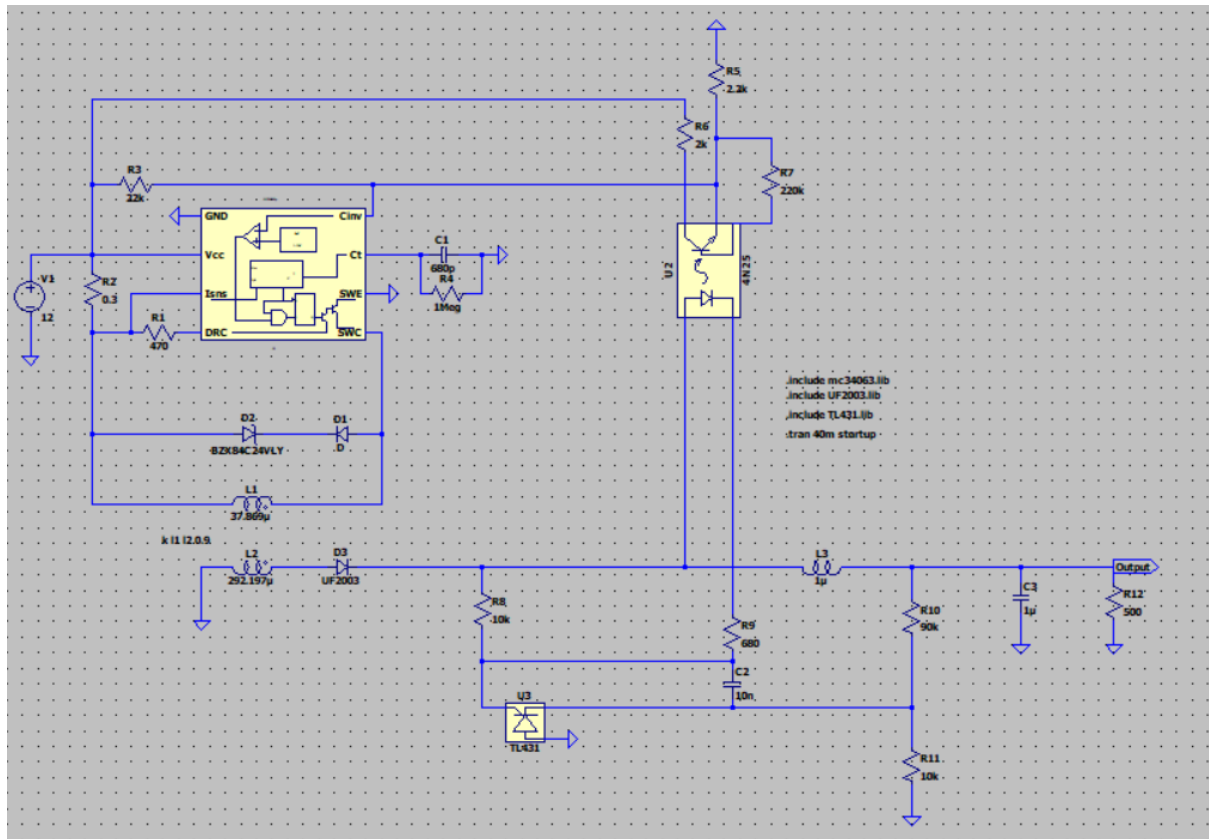


Figure 4: Flyback Converter Circuit

Simulation and Results

The output voltage startup transient of 12V to 25V converter is shown in Figure 5 with an output capacitor of $1\mu\text{F}$ and a load resistor of 500Ω . The output value of the converter is observed as 25.85V, which satisfies the required output voltage.

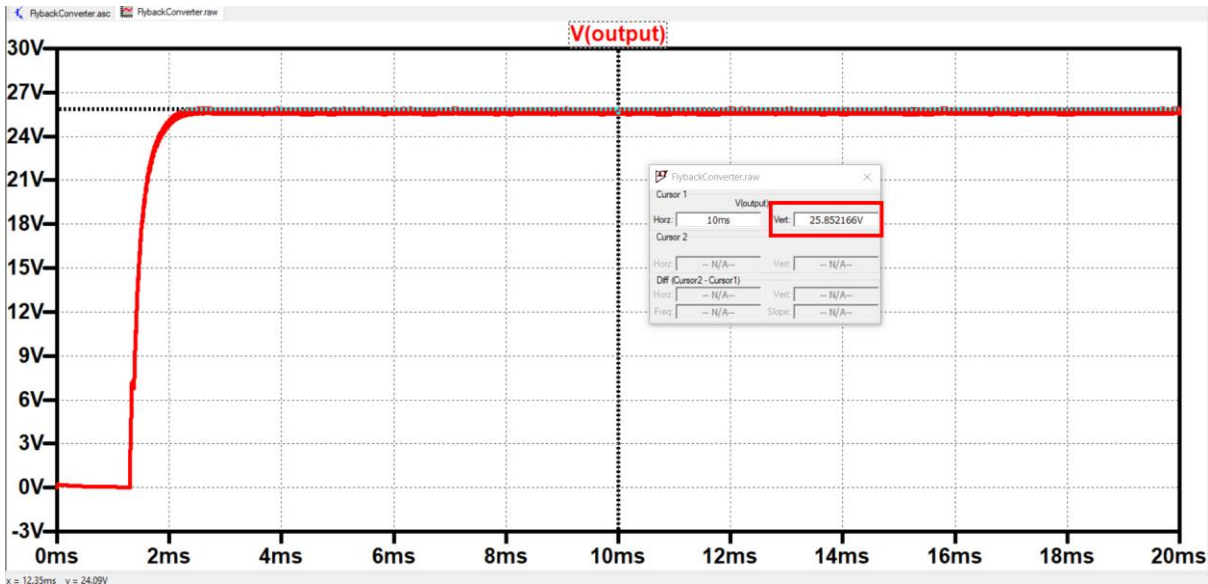


Figure 5: Output Voltage of Flyback Converter

The average output and input power is found through LTSpice as shown in Figure 6 and Figure 7, respectively.

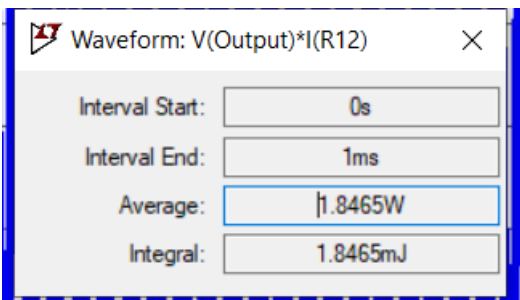


Figure 6: Average Value of Output Power

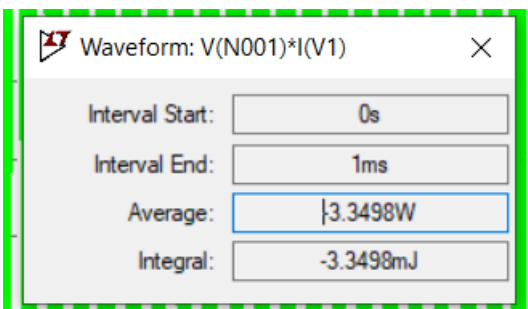


Figure 7: Average Value of Input Power

Hence the efficiency of the converter is calculated as 55.2%.

The zoomed-in version of the output voltage for one ripple period is shown in Figure 8. The ripple voltage value of the converter is shown in Figure 9.

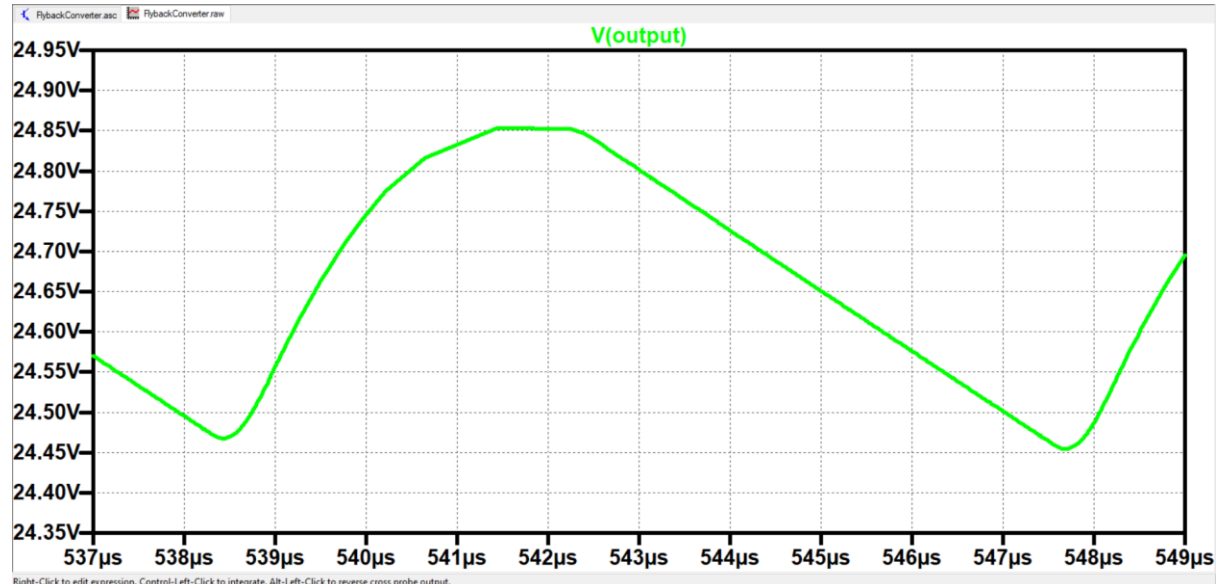


Figure 8: Output Voltage for One Ripple Period

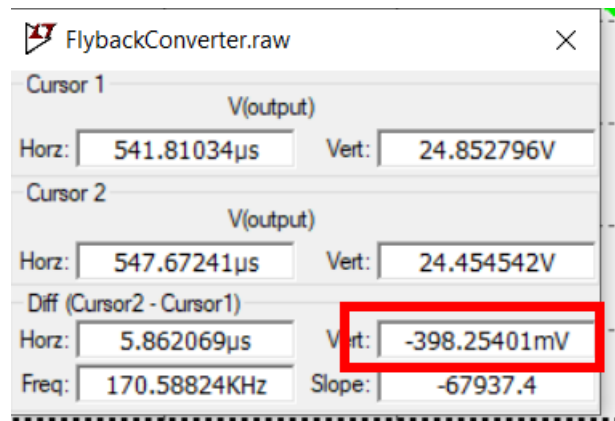


Figure 9: The Ripple Voltage Value

This simulated ripple voltage can be reduced by implementing larger output capacitor.

The switch voltage at pin1 with $V_d = 12\text{V}$ and $V_{\text{OR}} = 9\text{V}$ is shown in Figure 10.

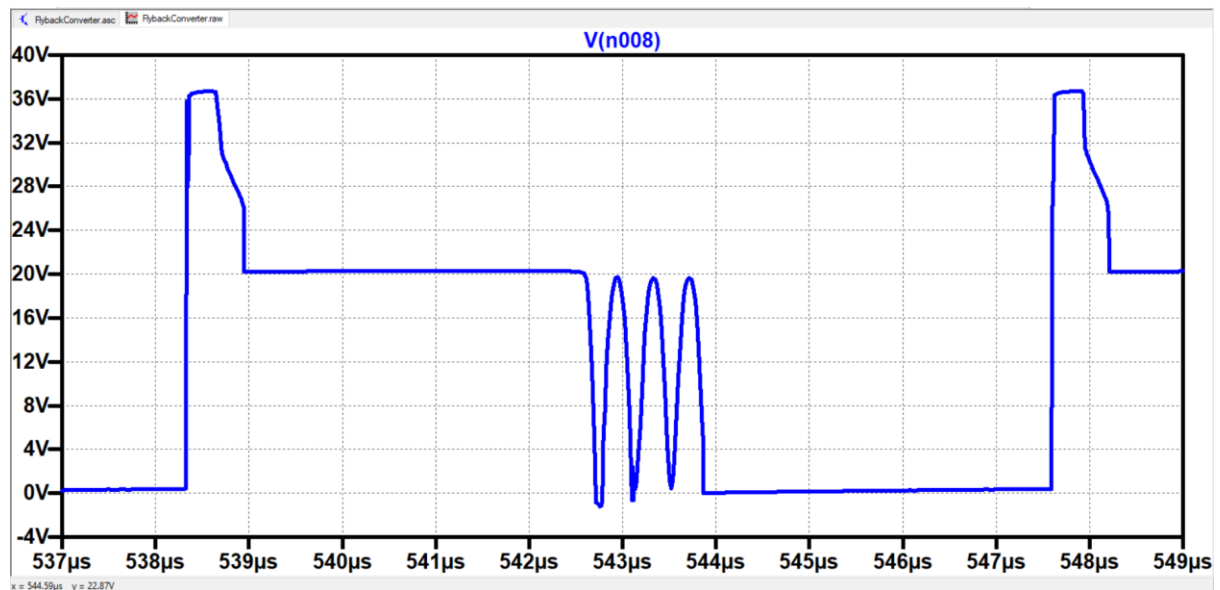


Figure 10: The Switch Voltage

The period of the converter is shown in Figure 11.

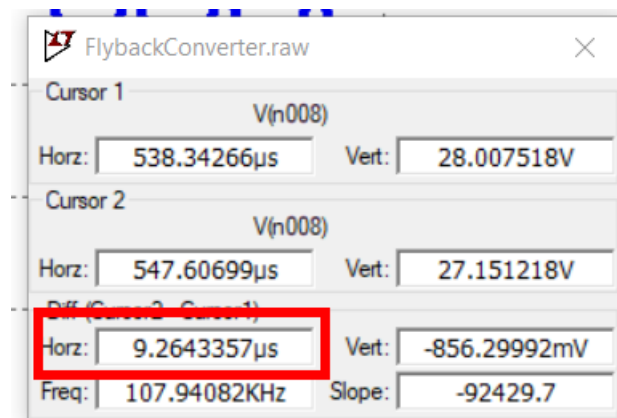


Figure 11: Period of the Converter

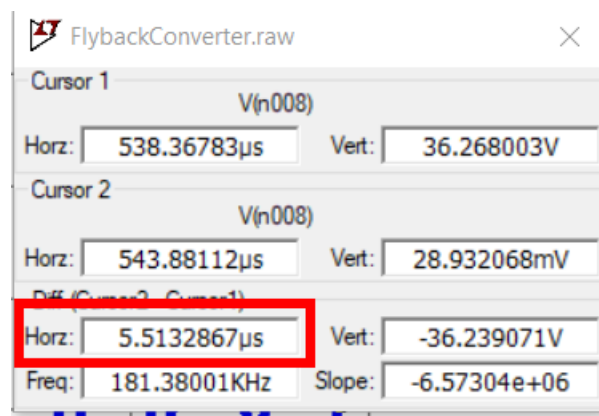


Figure 12: T_{OFF} Value of the Converter

These time values are quite close to the calculated values hence the value of the timing capacitor which is found by trial-and-error method is assumed to be correct.

Switch ON time is shown in Figure 13.

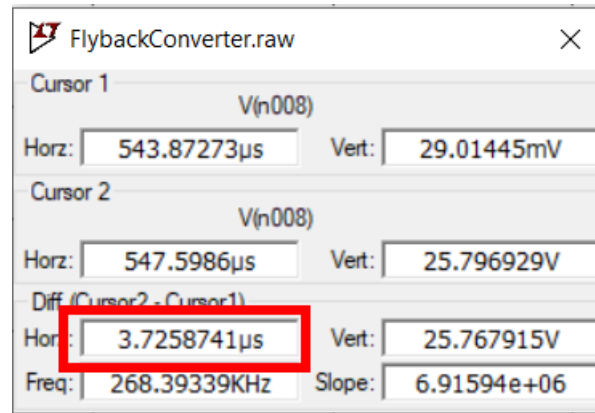


Figure 13: Switch ON Time Value

Transformer Implementation

For the implementation of the transformer E core E19 is used. Since the number of turns of the primary is found approximately 15, the inductor is wound, and the value of the inductor is measured as shown in figure 14.

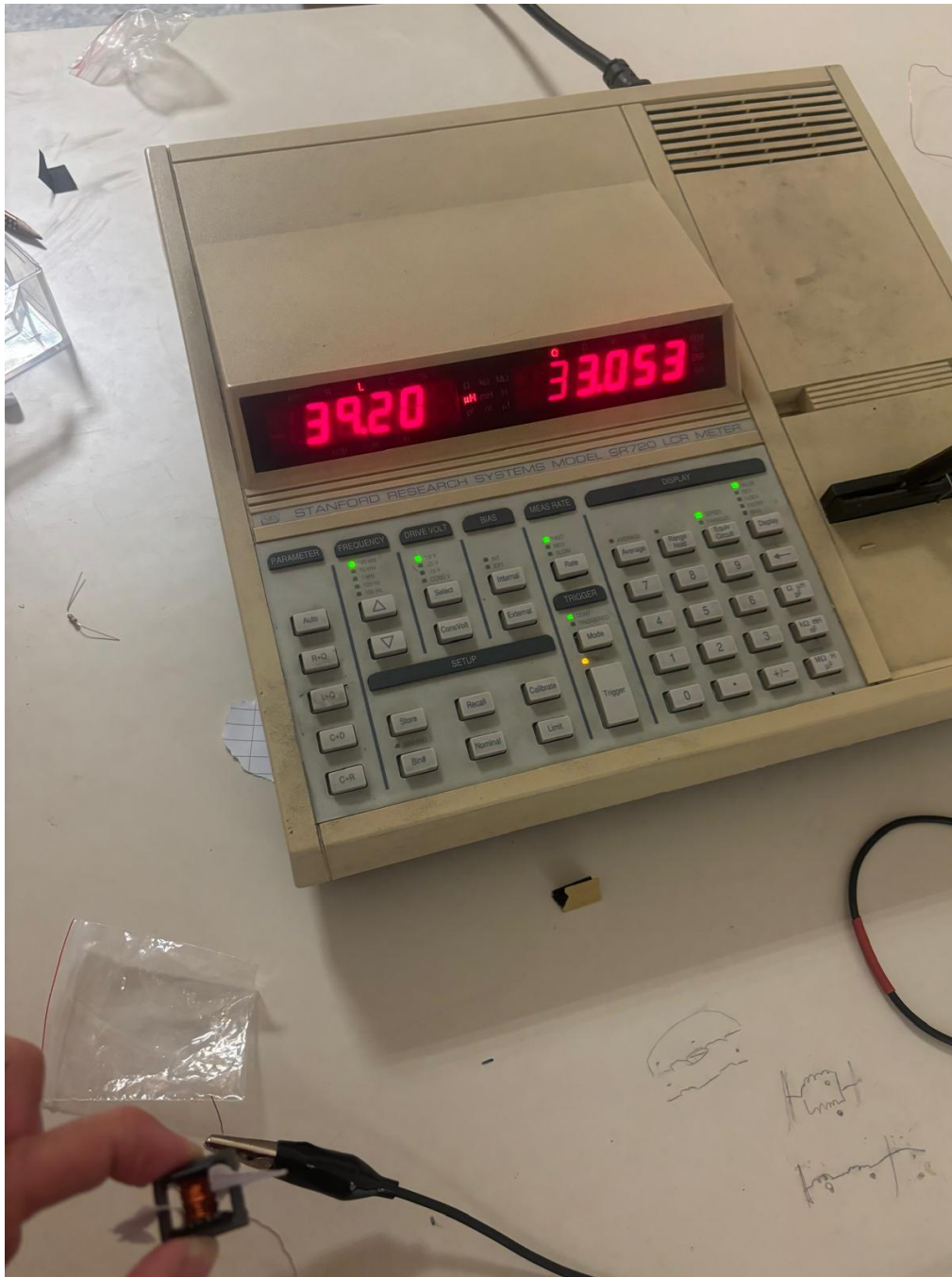


Figure 14: Inductance Value of the Primary at 100kHz

As shown above, the inductance value is quite close to the simulation value which is approximately $38\mu\text{H}$.

The value of the series resistance of the inductor is shown in figure 15.



Figure 15: Series Resistance Value of the Primary

The value of the inductance of the secondary is shown in figure 16. As shown in the figure the found inductance is quite close to the one used in the simulation which is $292\mu\text{H}$.

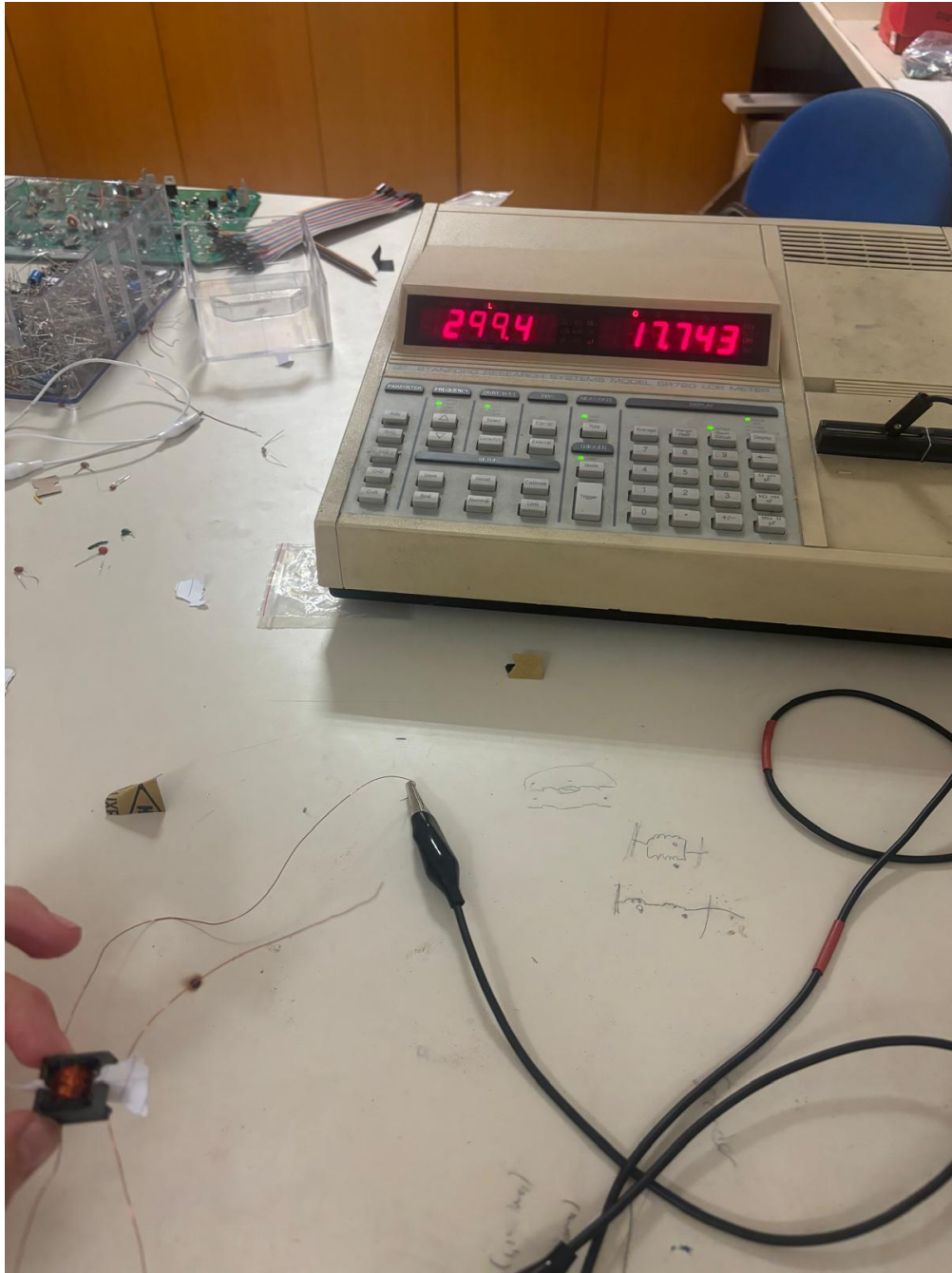


Figure 16: Inductance Value of the Secondary at 100kHz

The series resistance value of the secondary is shown in figure 17.



Figure 17: Series Resistance Value of the Secondary

The mutual inductance of the transformer is found as $91.7\mu\text{H}$. Hence the coupling coefficient is calculated as

$$k = \frac{M}{\sqrt{L_1 L_2}} = 0.92$$

Hence the experimental value of the coupling coefficient formula is found.

Conclusion

In conclusion, the design and analysis of the flyback converter's key components, including the primary and secondary inductance calculations, transformer winding, and component selection, have been successfully completed. The primary design objectives, such as achieving the target output voltage and maintaining discontinuous mode operation, guided the choice of parameters like the turns ratio, duty cycle, and switching period. Initial measurements of the transformer's inductance, series resistance, and coupling coefficient confirm that the design meets the theoretical specifications, providing a solid foundation for subsequent stages. This groundwork paves the way for PCB design and practical implementation, with the expectation that further optimization and testing will enhance the converter's efficiency and stability in real-world conditions.

References

[1] "Flyback converter," *Wikipedia*, Oct. 19, 2023. [Online]. Available: https://en.wikipedia.org/wiki/Flyback_converter. [Accessed: Nov. 12, 2024].